



**FIGURE B.10.3** A fi nite-state machine is implemented with a state register that holds the current stateand a combinational logic block to compute the next state and output functions. The latter two functions are often split apart and implemented with two separate blocks of logic, which may require fewer gates.