



**FIGURE B.8.3 Operation of a D latch, assuming the output is initially deasserted.** When the clock, *C*, is asserted, the latch is open and the *Q* output immediately assumes the value of the *D* input.