



FIGURE B.5.6 A 1-bit ALU that performs AND, OR, and addition (see Figure B.5.5 ).