

| ALUOp | | Function code fields | | | | | |
|--------|--------|----------------------|----|----|----|----|----|
| ALUOp1 | ALUOp0 | F5 | F4 | F3 | F2 | F1 | F0 |
| 0 | 1 | X | X | X | X | X | X |
| 1 | X | X | X | X | X | 1 | X |

a. The truth table for Operation2 = 1 (this table corresponds to the second to left bit of the Operation field in Figure D.2.1)

| ALUOp | | Function code fields | | | | | |
|--------|--------|----------------------|----|----|----|----|----|
| ALUOp1 | ALUOp0 | F5 | F4 | F3 | F2 | F1 | F0 |
| 0 | X | X | X | X | X | X | X |
| X | X | X | X | X | 0 | X | X |

b. The truth table for Operation1 = 1

| ALUOp | | Function code fields | | | | | |
|--------|--------|----------------------|----|----|----|----|----|
| ALUOp1 | ALUOp0 | F5 | F4 | F3 | F2 | F1 | F0 |
| 1 | X | X | X | X | X | X | 1 |
| 1 | X | X | X | 1 | X | X | X |

c. The truth table for Operation0 = 1

FIGURE D.2.2 The truth tables for three ALU control lines. Only the entries for which the output is 1 are shown. The bits in each field are numbered from right to left starting with 0; thus F5 is the most significant bit of the function field, and F0 is the least significant bit. Similarly, the names of the signals corresponding to the 4-bit operation code supplied to the ALU are Operation3, Operation2, Operation1, and Operation0 (with the last being the least significant bit). Thus the truth table above shows the input combinations for which the ALU control should be 0010, 0001, 0110, or 0111 (the other combinations are not used). The ALUOp bits are named ALUOp1 and ALUOp0. The three output values depend on the 2-bit ALUOp field and, when that field is equal to 10, the 6-bit function code in the instruction. Accordingly, when the ALUOp field is not equal to 10, we don't care about the function code value (it is represented by an X). There is no truth table for when Operation3=1 because it is always set to 0 in Figure D.2.1. See Appendix B for more background on don't cares.