FIGURE B.5.1 The 1-bit logical unit for AND and OR.